

Enrolment No: E2205FV0827 Name of Student: MADHAV GUPTA

MID-TERM EXAMINATION EVEN SEMESTER 2022-23

COURSE CODE	CSET102	MAX. DURATION	1 HRS
COURSE TITLE	INTRODUCTION TO ELECTRICAL AND ELECTRONICS		
COURSE CREDIT	5	TOTAL MARKS	20

- 1) Find the voltage V_{ab} and the current i_0 in the circuit shown in Figure 1.

(6 Marks)

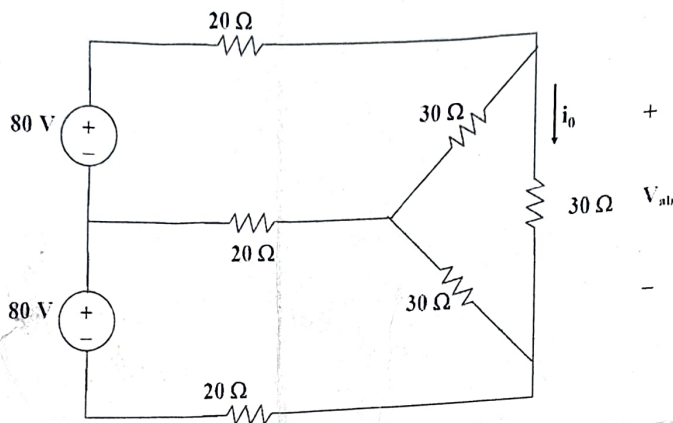


Figure 1

- 2) For the circuit shown in Figure 2, determine the power consumed by the 5Ω resistor.

(3 Marks)

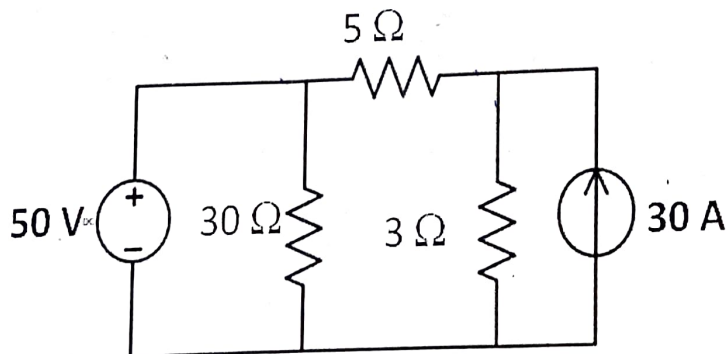


Figure 2

- 3) Determine the current through the 6Ω resistor for the circuit shown in Figure 3. (2 Marks)

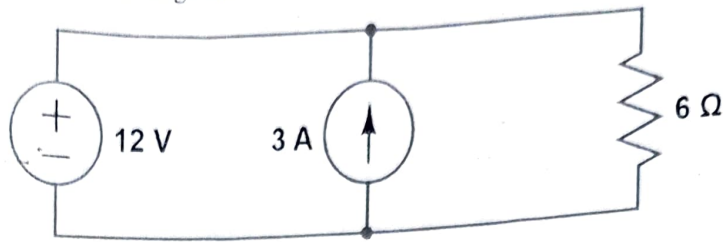


Figure 3

- 4) Replace the circuit between nodes *A* and *B* in Figure 4 with a voltage source in series with a single resistor. Determine the open circuit voltage in the simplified circuit. (5 marks)

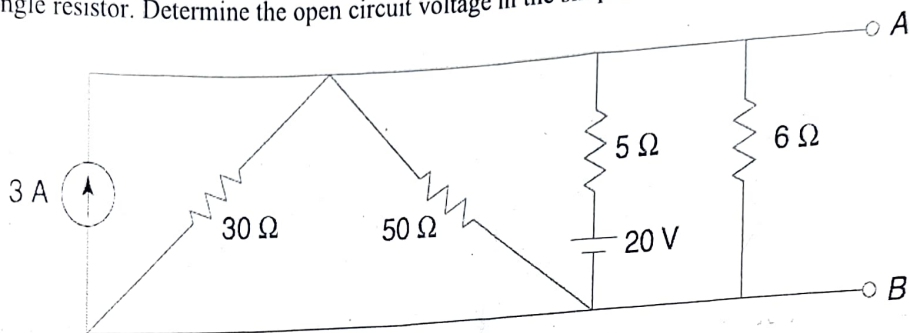


Figure 4

- 5) Simplify the circuit shown in Figure 5 using Thevenin's theorem. The load resistance is connected between nodes *A* and *B*. Find the voltage across the load resistor and the current flowing through the load resistor. (4 Marks)

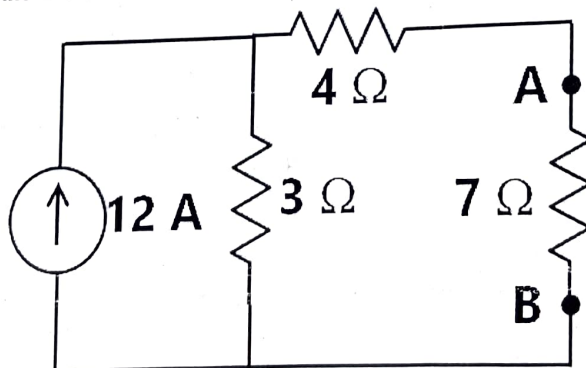


Figure 5

END OF QUESTION PAPER