



Enrollment No.: E22GDU0827 Name: MADHAN

Department/School: SCSET

### End Semester Examination, Even Semester 2022-23

Course Code: CSET-105

Max. Time Duration: 2 hour

Course Name: Digital Design

Max. Marks: 35

WRITE YOUR BATCH NUMBER ON THE TOP OF FRONT PAGE OF YOUR ANSWERSHEET


#### Instructions:

- Do not write anything on the question paper except name, enrolment number and school.
- Carrying mobile phone, smart watch and any other non-permissible materials in the examination hall is an act of UFM.
 
#### 1. Attempt all the questions.

(1 \* 5 = 5 Marks)


- Write the truth table of 4:2 Priority Encoder.
- Draw D flip flop in toggle mode.
- Draw a circuit that removes Race around condition in JK flip flops.
- What is the difference between Mealy and Moore state machines?
- Calculate the output Y in the below circuit


 
#### 2. Attempt all the questions.

(3\*5 = 15 Marks)

- Adi needs JK flip-flops in order to make an application specific circuit. By fault, he bought D-Flip Flops from the market. Help Adi to use D-Flip Flops as JK.
- Adi wants to code a three-bit binary number into its corresponding Gray code. Help Adi in forming the truth table of the conversion and then in implementing the circuit.
- Can more than one decoder output be activated at one time? Justify your answer with an example circuit using 2:4 Decoders.
- Design Mod-8 asynchronous UP counter using T-Flip Flops. Also explain its working using truth table and timing diagram.
- Four rectangular LEDs a, b, c and d are arranged in square pattern on a board. Consider an anonymous 2:4 decoding in which the four outputs correspond to four different states of LEDs (i), (ii), (iii) and (iv) as shown in figure below. Realize this circuit using fundamental gates.



→ OFF

→ ON

(LED ON/OFF)

3. Attempt all the questions.

(5\*3 = 15 Marks)

a. What are Shift Registers. List the various types of Shift Registers. Draw and explain the working of Universal Shift Register.

b. What is a PLD and how a PAL differs from PLA? Realize the following Boolean expressions in its minimized form using a single PLA.


$$F_1(A, B, C) = (1, 2, 4, 6, 7) \text{ and}$$

$$F_2(A, B, C) = (3, 5, 6, 7)$$

*F corresponding to  $\Sigma$*

*→ Minterms, not Maxterms*

 c. Design the counter that goes through below state diagram using T-flip-flops. Also explain its working using truth table and timing diagram.



— x — x — x — x — x — x — x — x — x — x —